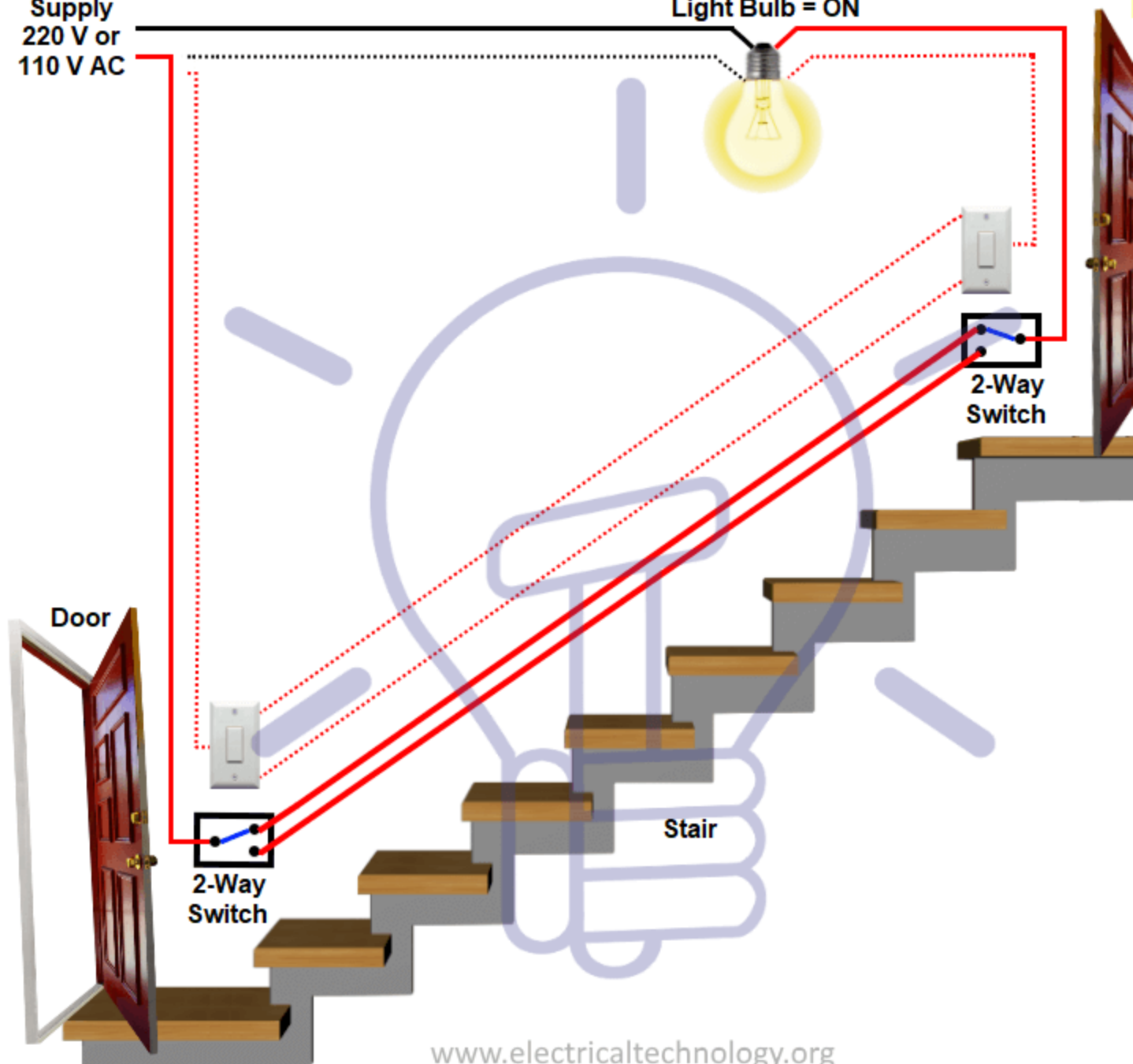


Earth's Omitted For Clarity

Supply  
220 V or  
110 V AC


Light Bulb = ON




[www.electricaltechnology.org](http://www.electricaltechnology.org)
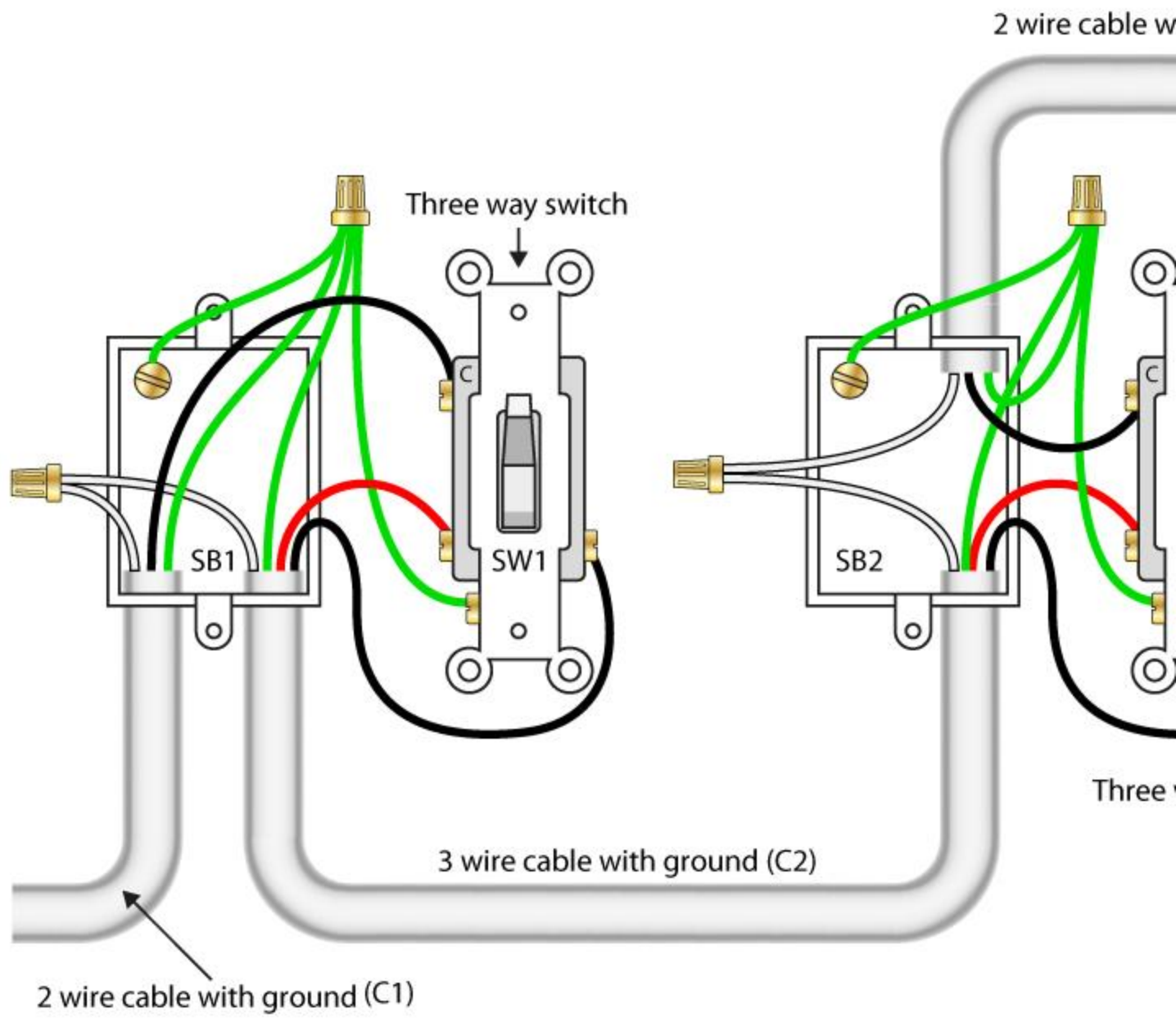
## Staircase Wiring Circuit Diagram

How to Control a Lamp from Two Different Places by Two 2-Way Switches



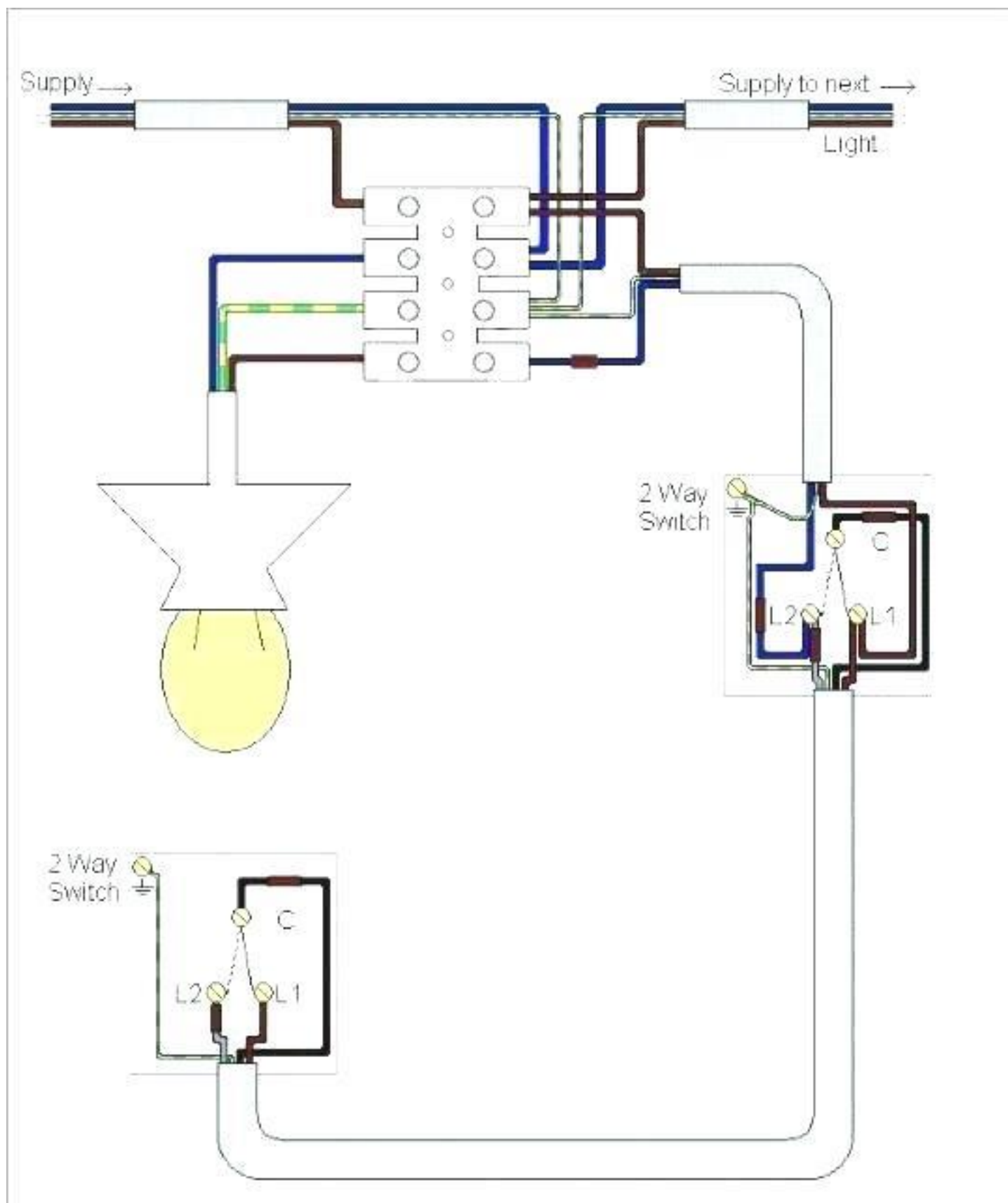

Protective earth  
conductors  
omitted for clarity

Multiple lamps  
switched

Lights switch from multiple  
locations using a pair of two  
way switches, and any  
number of additional  
intermediate switches

